

Step 1 : Determine mux size

Ersin Alan

1801062642

Alan

load, swap, clear (load all 0s)


4 operations: above, plus maintain, present value.

- Use 4×1 mux

Step 2 : Create mux operation table

S_1	S_0	Operations
0	0	maintain present value.
0	1	Clear
1	0	Load
1	1	Swap

Step 3 : Connect mux input

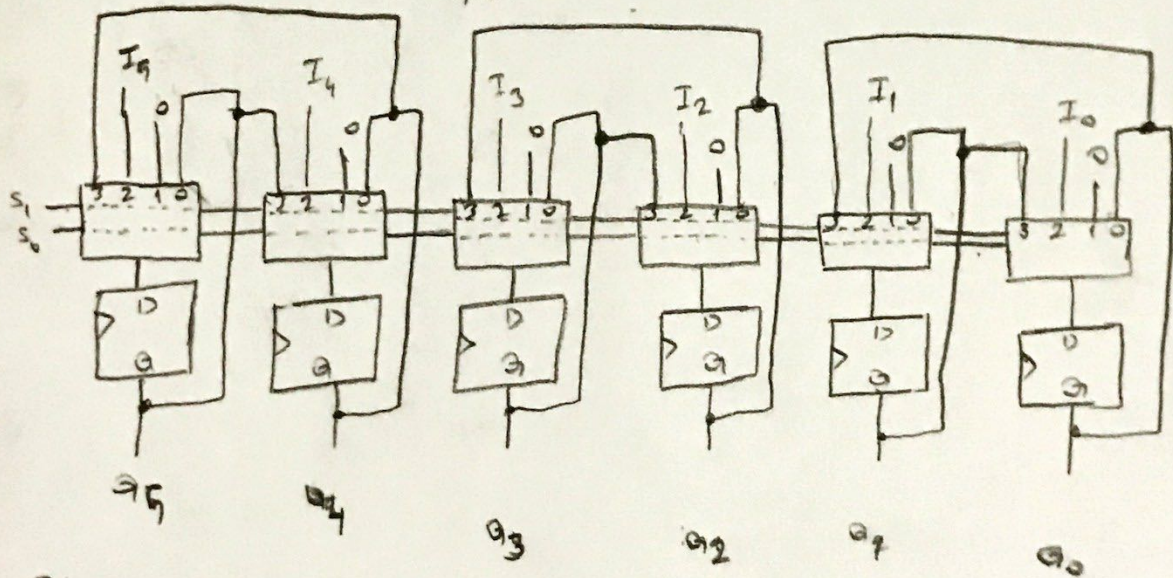

Step 4: Map control lines

Input	control lines			output	
	clr	load	swap	Q_1	Q_0
0	0	0	0	0	0
1	0	0	0	0	1
X	1	0	0	1	0
X	X	X	1	1	1

Operation

maintain present value

clear

load

swap

$$Q_1 = \text{load} + \text{swap}' + \text{swap}$$

$$Q_0 = \text{clr} + \text{load}' + \text{swap}' + \text{swap}$$